

2009

EE : Electrical Engineering


AI24BTECH11022 - Pabbuleti Venkata Charan Teja




49) An average-reading digital multimeter reads 10V when fed with a triangular wave, symmetric about the time-axis. For the same input an rms-reading meter will read

a) $\frac{20}{\sqrt{3}}$
b) $\frac{10}{\sqrt{3}}$


c) $20\sqrt{3}$
d) $10\sqrt{3}$

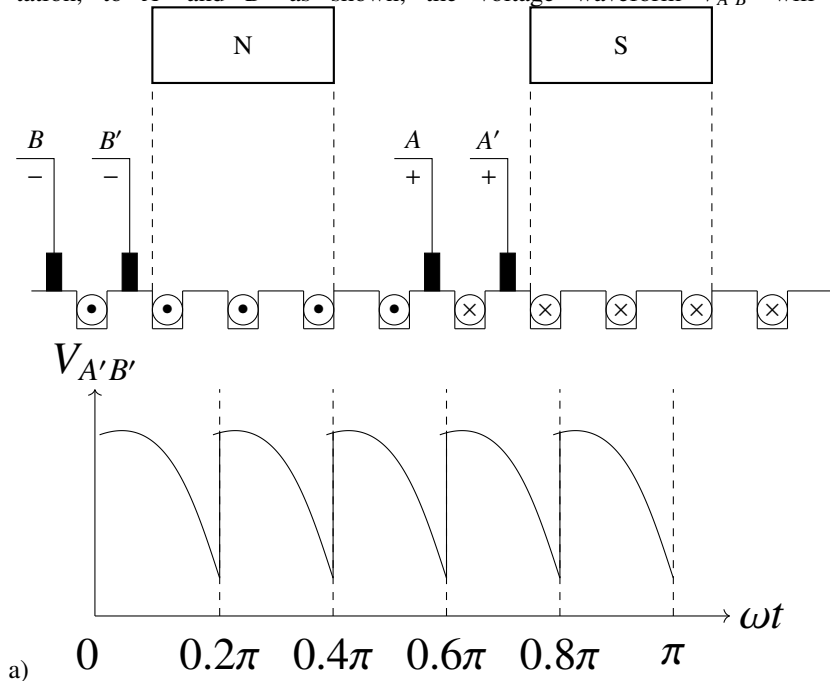50) Figure shows the extended view of a 2 pole dc machine with 10 armature conductors. Normal brush positions are shown by A and B , placed at the interpolar axis. If the brushes are now shifted, in the direction of rotation, to A' and B' as shown, the voltage waveform $V_{A'B'}$ will resemble



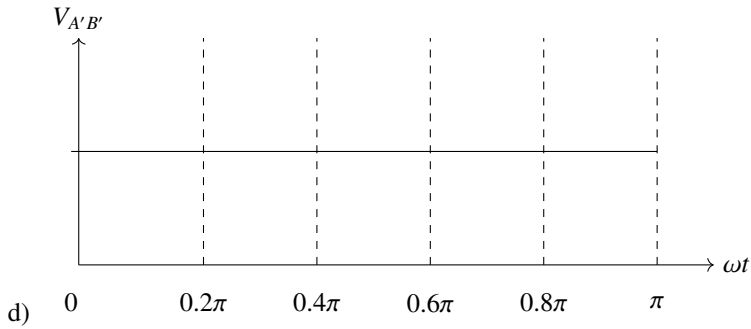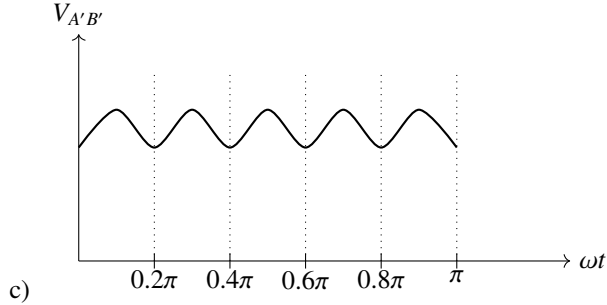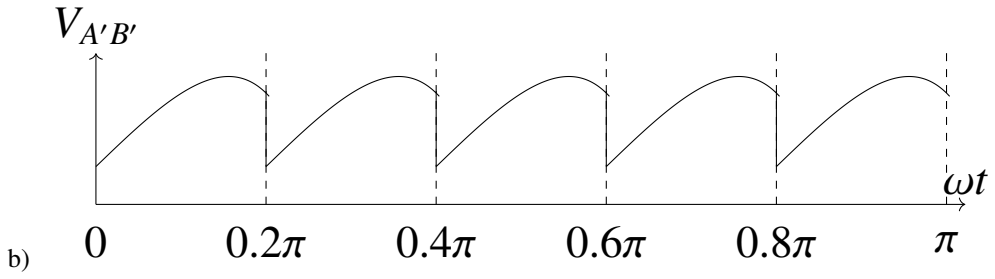

Common Data for Questions 51 and 52 :

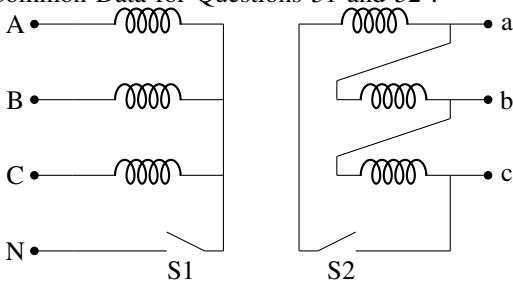

The star-delta transformer shown above is excited on the star side with a balanced, 4 – wire, 3 – phase, sinusoidal voltage supply of rated magnitude. The transformer is under no load condition.

51) With both $S1$ and $S2$ open, the core flux waveform will be


- a) a sinusoid at fundamental frequency c) peaky with third-harmonic
b) flat-topped with third harmonic d) none of these

52) With $S2$ closed and $S1$ open, the current waveform in the delta winding will be

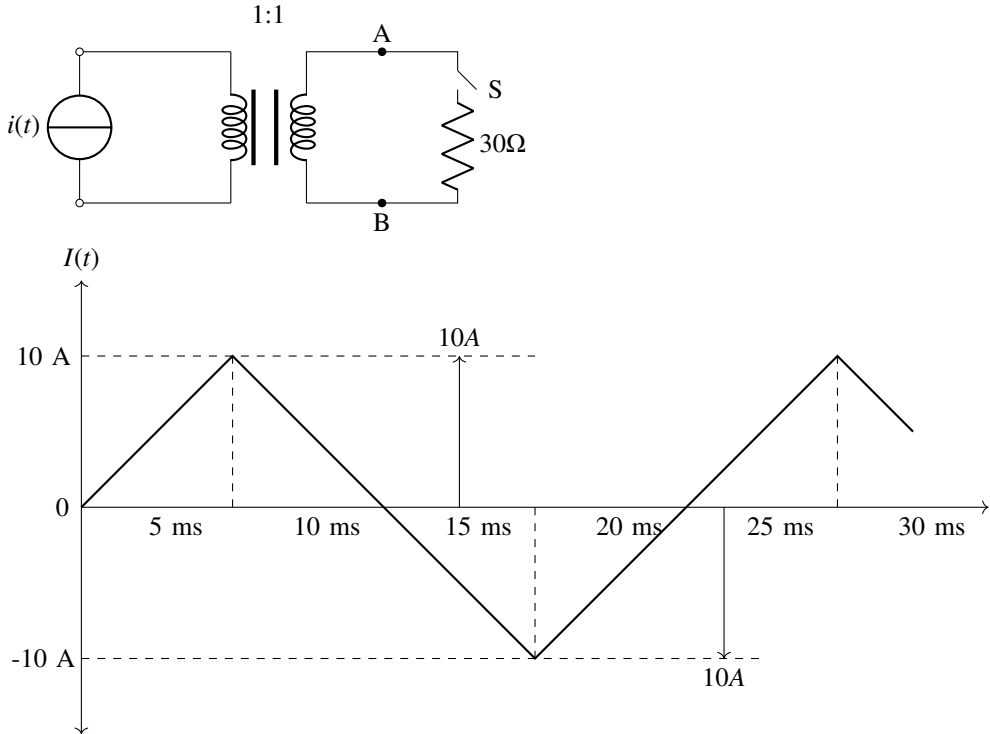- a) a sinusoid at fundamental frequency c) only third-harmonic
b) flat-topped with third harmonic d) none of these

Common Data for Questions 53 and 54 :

The circuit diagram shows a two-winding, lossless transformer with no leakage flux, excited from a current source, $i(t)$, whose waveform is also shown. The transformer has a magnetizing inductance of $\frac{400}{\pi} \text{ mH}$.



53) The peak voltage across A and B, with S open is

- a) $\frac{400}{\pi} \text{ V}$ c) $\frac{4000}{\pi} \text{ V}$
b) 800 V d) $\frac{800}{\pi} \text{ V}$

54) If the waveform of $i(t)$ is changed to $i(t) = 10 \sin 100\pi t \text{ A}$, the peak voltage across A and B with S closed is

- a) 400V
b) 240V
c) 320V
d) 160V

Common Data for Questions 55 and 56:

A system is described by the following state and output equations

$$\frac{dx_1(t)}{dt} = -3x_1(t) + x_2(t) + 2u(t)$$

$$\frac{dx_2(t)}{dt} = -2x_2(t) + u(t)$$

$$y(t) = x_1(t)$$

where $u(t)$ is the input and $y(t)$ is the output


55) The system transfer function is

- a) $\frac{s+2}{s^2+5s-6}$ c) $\frac{2s+5}{s^2+5s+6}$
b) $\frac{s+3}{s^2+5s+6}$ d) $\frac{2s-5}{s^2+5s-6}$

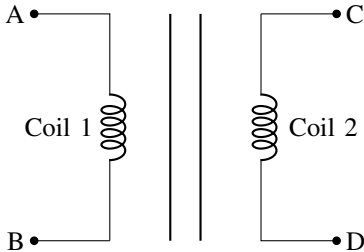56) The state-transition matrix of the above system is

- $$\begin{array}{ll} \text{a)} & \begin{bmatrix} e^{-3t} & 0 \\ e^{-2t} + e^{-3t} & e^{-2t} \\ e^{-3t} & e^{-2t} - e^{-3t} \end{bmatrix} \\ \text{b)} & \begin{bmatrix} e^{-3t} & e^{-2t} - e^{-3t} \\ 0 & e^{-2t} \end{bmatrix} \end{array} \qquad \begin{array}{ll} \text{c)} & \begin{bmatrix} e^{-3t} & e^{-2t} + e^{-3t} \\ 0 & e^{-2t} \\ e^{3t} & e^{-2t} - e^{-3t} \end{bmatrix} \\ \text{d)} & \begin{bmatrix} e^{3t} & e^{-2t} - e^{-3t} \\ 0 & e^{-2t} \end{bmatrix} \end{array}$$

Statement for Linked Answer Questions 57 and 58 :



The figure above shows coils 1 and 2, with dot markings as shown, having 4000 and 6000 turns respectively. Both the coils have a rated current of 25A. Coil 1 is excited with single phase, 400V, 50Hz supply.


57) The coils are to be connected to obtain a single phase, 400/1000V, auto-transformer to drive a load of 10kVA. Which of the options given should be exercised to realize the required auto-transformer?

- a) Connect A and D ; Common B c) Connect A and C ; Common B
 b) Connect B and D ; Common C d) Connect A and C ; Common D

58) In the autotransformer obtained in Question 57, the current in each coil is

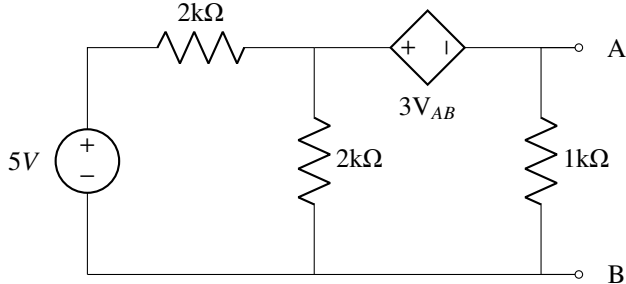- a) Coil-1 is 25A and Coil-2 is 10A c) Coil-1 is 10A and Coil-2 is 15A
 b) Coil-1 is 10A and Coil-2 is 25A d) Coil-1 is 15A and Coil-2 is 10A

Statement for Linked Answer Questions 59 and 60 :



59) For the circuit given above, the Thevenin's resistance across the terminals A and B is

- a) $0.5k\Omega$ c) $1k\Omega$
 b) $0.2k\Omega$ d) $0.11k\Omega$

60) For the circuit given above, the Thevenin's voltage across the terminals A and B is

- a) 1.25 V c) 1 V
 b) 0.25 V d) 0.5 V